

CHAPTER 9: CURRENT AND RESISTANCE

MIDTERM 2

ANDREA ACOSTA
20607848

$$\textcircled{1} (a) \tau = RC \Rightarrow C = \tau/R = (100 \times 10^{-6} \text{ s}) / (1.00 \times 10^3 \Omega) = \boxed{1 \times 10^{-7} \text{ F} = C_{\max}}$$

(b) NO it is not difficult in practice to limit the capacitance to less than $C_{\max} = 1 \times 10^{-7} \text{ F}$ because it is an ECG monitor and can measure at time constant less than $100 \mu\text{s}$

$$(c) V = V_0 (1 - e^{-t/RC}) \Rightarrow 30 = 60 (1 - e^{-t/100 \times 10^{-6}})$$

$$\Rightarrow \frac{30}{60} = e^{-t/100 \times 10^{-6}} \Rightarrow \ln \frac{0.5}{0.5} = \ln e^{-t/100 \times 10^{-6}} = 0.6931 = \frac{t}{100 \times 10^{-6}} \Rightarrow \boxed{t = 6.93 \times 10^{-5} \text{ s}}$$

$$\textcircled{2} (a) \Phi = 0 \text{ then } V(t) = V_0 \sin(2\pi ft)$$

$$\frac{V_0}{\sqrt{2}} \sin(2\pi ft) = 0$$

$$\sin(2\pi ft) = 0$$

$$\sin(2\pi ft) = 0$$

$$\sin(2\pi ft) = \sin(\pi)$$

$$2\pi ft = \pi$$

$$t = \frac{\pi}{2\pi f} = \frac{\pi}{2\pi (60 \text{ Hz})} = 0.00833 = \boxed{8.33 \times 10^{-3} \text{ s} = 8.33 \text{ ms}}$$

$$(b) P_{\max} = \frac{V_0^2}{R} = \frac{(120 \text{ V})^2}{10^3 \Omega} = \boxed{14.4 \text{ W}}$$

$$(c) P_{\text{avg}} = \frac{V_0^2}{2R} = \frac{(120 \text{ V})^2}{2(10^3 \Omega)} = \boxed{7.2 \text{ W}}$$

$$\textcircled{3} P = VI = 110 \text{ V} \cdot 3.00 \text{ A} = 330 \text{ W, refrigerator}$$

$$P_{\text{total}} = (330 \text{ W} + 100 \text{ W} + 60 \text{ W} + 3.0 \text{ W}) = 493 \text{ W}$$

$$\begin{aligned} 493 \text{ W} \times \frac{12 \text{ hours}}{1 \text{ day}} \times \frac{30 \text{ days}}{1 \text{ month}} &= 177480 \text{ watt-hours} \\ &= \frac{177480 \text{ watt-hours}}{10^3 \text{ W}} = 177.48 \text{ kWh} \\ &= 177.48 \text{ kWh} \times \frac{\$0.22}{1 \text{ kWh}} \\ &= 35.496 \approx \boxed{\$35.50} \end{aligned}$$

CHAPTER 10: DIRECT-CURRENT (DC) CIRCUITS

① $\frac{1}{R_{eq}} = \frac{1}{2R} + \frac{1}{2R} \Rightarrow R_{eq} = R$ where $R = 1k\Omega$
 $V = 12V$

Junction rule $I_2 + I_3 = I_1$
 $12 - I_2 R - I_3 R = 0$
 $12 - I_2 R - I_1 R = 0$
 $12 - I_2 R - I_2 R = 0$
 $12 = 2000 I_2$
 $I_2 = 6mA$

Loop 1 $12 = 1000 I_1 + 1000 I_2$
 $12 - 1000 I_3 - 1000 I_1 = 0$
 $12 = 1000 I_1 + 1000 I_2$
 $12 = 2000 I_1 - 1000 I_2$
 $24 = 3000 I_1 \Rightarrow I_1 = \frac{24}{3000} = 0.008A = 8mA$

$1000 I_2 = 2000 I_1 - 12$
 $1000 I_2 = 2000 \times 8 \times 10^{-3} - 12$
 $I_2 = 4mA$

$I_3 = I_1 - I_2$
 $= 8mA - 4mA = 4mA = I_3$

Power: $P = I_1^2 R + I_2^2 R + I_3^2 R$
 $= [(8 \times 10^{-3})^2 \times 1000] + [(4 \times 10^{-3})^2 \times 1000] + [(4 \times 10^{-3})^2 \times 1000] W$
 $= 0.096 W = 96 mW = \text{power consumed in resistors}$

② (a) $\mathcal{E} - I_1 r - (I_1 + I_2) R = 0$ where $\mathcal{E} = 1.5V$, $r = 0.25\Omega$, $R = 50\Omega$

$1.5V = 0.25\Omega I_1 + 50I_1 + 50I_2$

$\mathcal{E} - I_1 r + I_2 r - \mathcal{E} = 0$

$-I_1 r + I_2 r = 0$

$-I_1 + I_2 = 0$
 $+I_1 \quad +I_2$

$\Rightarrow I_2 = I_1 = I$

$1.5V = 0.25I + 100I$

$1.5V = 100.25I$

$I = \frac{1.5V}{100.25} = 0.01496A \times 2 = 0.0299A \approx 0.03A = I$

(b) $i = \frac{q}{t} \Rightarrow t = \frac{q}{i} = \frac{2(2.5A \text{ hrs})}{0.03A} = 166.67 \text{ hrs} \approx 167 \text{ hrs} = 600,000 \text{ secs}$
 $\times 3600$

total current + total charge.

CHAPTER 11: MAGNETIC FORCES AND FIELDS


① (a) If the particle bends toward left then the velocity must point vertically upwards. If \vec{B} is into the page too and given the Lorentz equation ($\vec{F} = q(\vec{v} \times \vec{B})$), the charge q of the particle has to be positive because \vec{F} points left.

(b) If the particle had the mass of an electron what's strange is that an electron is negatively charged. With this negative charge the particle should turn right when entering the magnetic field. Thus what's strange is that although the same mass as an electron the particle follows a different path because it is positively charged unlike an electron.

(c) $|\vec{F}| = qvB \sin \theta$

$$|\vec{F}| = qvB \sin 90^\circ$$

$$|\vec{F}| = (1.602 \times 10^{-19}) (10^6) (0.05) = \boxed{8.01 \times 10^{-15} \text{ N}}$$

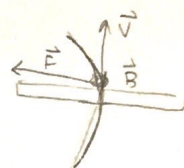

If \vec{v} is vertically upwards & \vec{B} is into the page, by $\vec{F} = q(\vec{v} \times \vec{B})$ & that q is positive, \vec{F} has to be horizontally leftwards after crossing the lead plate (or $-x$ axis).