

2: Current and Resistance

$$\textcircled{1} \tau = RC, \tau < 100 \text{ ms}, R = 1 \text{ k}\Omega$$

$$< 1 \times 10^{-4} \text{ s} = 1 \times 10^3 \Omega$$

a)

$$RC < 1 \times 10^{-4} \text{ s}$$

$$\frac{1 \times 10^3 \cdot C}{1 \times 10^3 \Omega} < \frac{1 \times 10^{-4} \text{ s}}{1 \times 10^3 \Omega} \Rightarrow C < 1 \times 10^{-7} \text{ F}$$

$$\Rightarrow \boxed{C < 100 \text{ nF}}$$

b) No it wouldn't be difficult because the time constant is $\tau < 100 \text{ ms}$ therefore we can limit the capacitance to less than 100 nF .

$$\text{c) } R = 10^3 \Omega \quad E = 60 \text{ mV} \quad v = 30 \text{ mV} \quad RC = \tau = 1 \times 10^{-4}$$

$$V_C(t) = E(1 - e^{(-t/\tau)})$$

$$\Rightarrow 30 \text{ mV} = 60 \text{ mV}(1 - e^{(-t/10^{-4})})$$

$$\Rightarrow 30 \text{ mV} = 60 - 60 e^{(-t/10^{-4})}$$

$$\Rightarrow 0.5 = e^{(-t/10^{-4})} \Rightarrow \ln(0.5) = -\left(\frac{t}{10^{-4}}\right)$$

$$\Rightarrow 0.693 = \frac{t}{10^{-4}} \Rightarrow \boxed{t = 6.93 \times 10^{-5} \text{ s}}$$

2. $V(t) = V_0 \sin(2\pi ft + \phi)$, $f = 60\text{Hz}$ $V_0 = 120\text{V}$

a) $\phi = 0$ $V(t) = 120 \sin(120\pi t)$

$$V(t) = 0$$

$$0 = 120 \sin(120\pi t)$$

$$V(t) = 0 \text{ when } \rightarrow \sin(120\pi t) = 0$$

$$\sin(120\pi t) = 0 \text{ when } \rightarrow 120\pi t = n\pi$$

$$\Rightarrow t = \frac{n}{120}$$

$$\text{so } V(t) = 0 \text{ at } t = \frac{1}{120}\text{s}, t = \frac{2}{120}\text{s}, t = \frac{3}{120}\text{s} \dots \boxed{t = \frac{n}{120}\text{s}}$$

b) $P = IV$

$$P = I^2 R$$

$$P = \frac{V_0^2}{R}$$

$$P = \frac{120^2 \text{V}}{10^3 \Omega} = \frac{14400}{1000} = \boxed{14.4\text{W}}$$

c) Since its AC the formula would be

$$P = \frac{120^2 \text{V}}{2 \times 10^3 \Omega} = \boxed{7.2\text{W}}$$

$$3) P = 1V$$

$$P = 3(110) = 330W$$

$$\begin{aligned} \text{total Power} &= 330W + 100W + 60W + 3W = 163W + 330W \\ &= 493W \\ &= 0.493 \text{ kW} \end{aligned}$$

$$\text{Consumption per Day} = 0.493 \times 12 = 5.916 \text{ kW}$$

$$\text{Consumption per Month} = 5.916 \times 30 = 177.48 \text{ kW}$$


$$\text{Cost per Month} = 177.48 \times 0.2 = \boxed{35.50 \$}$$

3 Direct-Current Circuits

1.

$$R_{\text{tot}}^{-1} = R_1^{-1} + R_2^{-1} = \frac{1}{2R} + \frac{1}{2R} = \frac{2}{2R} = \frac{1}{R}$$

$$R_{\text{tot}} = R \quad \text{so,}$$

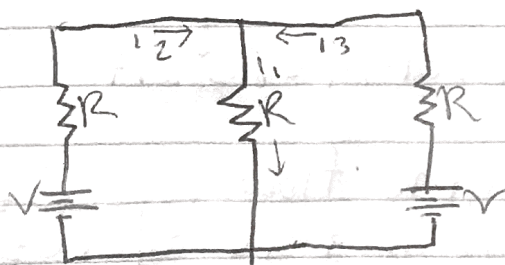

$$\frac{x-12}{1000 \Omega} + \frac{x}{1000 \Omega} + \frac{x-12}{1000 \Omega} = 0$$

$$\frac{3x}{1000} = \frac{24}{1000} \Rightarrow x = 8V$$

$$\boxed{i_1 = \frac{8}{1000} = 8 \text{ mA} \quad i_2 = \frac{12-8}{1000} = 4 \text{ mA} \quad i_3 = \frac{12-8}{1000} = 4 \text{ mA}}$$

1 Continued) $P = (i_1^2 + i_2^2 + i_3^2) R$

$$\Rightarrow (8^2 + 4^2 + 4^2) \times 10^{-6} \times 1000 = P$$

$$\Rightarrow \boxed{P = 0.096 \text{ W}}$$

2) $\epsilon = 1.5 \text{ V}$ $r = 0.25 \Omega$

a) loop 1:

$$i_1 r_1 - i_2 r_2 + E_1 + E_2 = 0$$

$$0.25 i_1 - 0.25 i_2 + 1.5 - 1.5 = 0$$

$$i_1 - i_2 = 0 \Rightarrow i_1 = i_2$$

loop 2: $I_2 r_2 + (I_1 + I_2) R - E_2 = 0$

$$0.25 i_2 + 2 i_2 (50) - 1.5 = 0$$

since $i_1 = i_2$

$$\Rightarrow 100.25 i_2 = 1.5$$

$$\Rightarrow i_2 = 0.0149 = 0.015 \text{ A}$$

So total current is $2 i_2$ since $i_1 = i_2$
so current flow = $\boxed{0.03 \text{ A}}$

b) $q = 2.5 \text{ A} \cdot \text{hr}$ $I = \frac{2q}{t} \Rightarrow t = \frac{2q}{I}$

$$\Rightarrow t = \frac{5}{0.03}$$

$$\Rightarrow \boxed{t = 166.667 \text{ hrs}}$$

4 Magnetic Forces and Fields

a) Q is positive as it corresponds with the right hand rule. The particle is moving upwards and that's the $+$ direction.

b) This is strange because the particle has the mass of an electron yet its behavior corresponds to a positive charged particle and as we know, electrons are negatively charged.

c) $B = 0.05 \text{ T}$ and $v = 10^6 \text{ m/s}$, $q = 1.6 \times 10^{-19} \text{ C}$
 $\theta = 90^\circ$

$$F = qvB \Rightarrow F = (1.6 \times 10^{-19}) (10^6) (0.05) \\ = (0.8 \times 10^{-14}) (10^6) \\ = 0.8 \times 10^{-13}$$

$$\boxed{F = 8 \times 10^{-14} \text{ N}}$$