

Chapter 9

1. a)

$$\text{time} = 100 \mu\text{s} \left(\frac{10^{-6} \text{s}}{1 \mu\text{s}} \right) = 0.0001 \text{ or } 1 \times 10^{-4}$$

$$\text{resistance} = 1.00 \text{ k}\Omega \left(\frac{10^3 \Omega}{1 \text{ k}\Omega} \right) = 1000 \text{ or } 1 \times 10^3$$

$$t = CR \Rightarrow C = t/r$$

$$C = \frac{1 \times 10^{-4}}{1 \times 10^3}$$

$$C = 1 \times 10^{-7} \text{ F} \rightarrow \text{maximum capacitance}$$

b) No, it would not be difficult to limit the capacitance.

c) $V(t) = V_0(1 - \exp(-t/\tau))$ & find t

$$\text{Known: } R = 1 \times 10^3 \quad V_0 = 60 \text{ mV} = 0.06 \text{ V} \quad V = 30 \text{ mV} = 0.03 \text{ V}$$

$$V = V_0(1 - \exp(-t/\tau)) \quad \tau = 1 \times 10^{-4}$$

$$0.03 = 0.06(1 - \exp(-t/1 \times 10^{-4}))$$

$$0.5 = 1 - \exp(-t/1 \times 10^{-4})$$

$$-0.5 = -\exp(-t/1 \times 10^{-4})$$

$$0.5 = \exp(-t/1 \times 10^{-4})$$

$$\ln(0.5) = \ln[\exp(-t/1 \times 10^{-4})]$$

$$-0.693 = \frac{-t}{1 \times 10^{-4}}$$

$$-6.931 \times 10^{-5} = -t$$

$$t = 6.931 \times 10^{-5}$$

2. a) $f = 60 \text{ Hz}$ $V_0 = 120 \text{ V}$ $\phi = 0$ $V(t) = 0$

$$V(t) = V_0 \sin(2\pi ft + \phi)$$

$$0 = 120 \sin(2\pi(60)t)$$

$$0 = \sin(120\pi t)$$

$\sin(\pi) = 0$ which means:

$$120\pi t = \pi$$

$$t = \frac{\pi}{120\pi} = \frac{1}{120}$$

$$t \approx 8.33 \times 10^{-3}$$

$$b) 1 \text{ k}\Omega \left(\frac{10^3 \Omega}{1 \text{ k}\Omega} \right) = 1 \times 10^3 \Omega$$

$$P_{\max} = \frac{V_0^2}{R} = \frac{(120)^2}{1 \times 10^3 \Omega} = \frac{1.44 \times 10^4}{1 \times 10^3} = \boxed{1.44 \times 10^1 \text{ watts}}$$

$$c) 1 \text{ k}\Omega \left(\frac{10^3 \Omega}{1 \text{ k}\Omega} \right) = 1 \times 10^3 \Omega$$

$$P_{\text{aver}} = \frac{1}{2} \frac{V_0^2}{R} = \frac{1}{2} (1.44 \times 10^1) = \boxed{7.2 \text{ watts}}$$

$$3. \text{ current} = 3.00 \text{ A} \quad \text{voltage} = 110 \text{ V} \quad \text{total Watts} = 100 \text{ W} + 60 \text{ W} + 3 \text{ W}$$

$$0.2 \frac{\text{kW}}{\text{hr}} \Rightarrow \frac{200 \text{ W}}{\text{hr}} \quad 12 \text{ hrs per day for one month.}$$

$$P = IV$$

$$P_{\text{total}} = (3 \cdot 110) + (100 + 60 + 3) \\ = 493 \text{ watts}$$

$$E_{\text{total}} = 493 \text{ W} \cdot 12 \text{ hr} \cdot 30 \text{ days} \\ = 1.7748 \times 10^5 \text{ W/hr} \Rightarrow 177.48 \text{ kW/hr} \\ = (177.48 \text{ kW/hr})(0.2 \text{ \$/kW/hr}) \\ = \$35.50 \text{ total cost}$$

Chapter 10

$$1. \text{ equations: } V - i_2 R - i_1 R = 0 \quad (1) \\ V - i_3 R - i_1 R = 0 \quad (2) \\ i_1 = i_2 + i_3 \quad (3)$$

since (1) & (2) both equal 0 then,

$$V - i_2 R - i_1 R = V - i_3 R - i_1 R \\ + i_2 R = + i_3 R$$

$$i_2 = i_3$$

knowing this then (3)

$$i_1 = i_2 + i_2$$

$$i_1 = 2i_2$$

$$V = 12 \text{ V} \quad R = 1 \text{ k}\Omega = 1000 \Omega$$

$$(1) \quad 12 - i_2(1000) - i_1(1000) = 0$$

$$1000(-i_2 - i_1) = -12$$

$$-i_2 - 2i_2 = \frac{-12}{1000}$$

$$-3i_2 = -0.012$$

$$i_2 = 0.004 \text{ A}$$

which also means $i_3 = 0.004 \text{ A}$
then

$$i_1 = 2i_2 \\ = 2(0.004)$$

$$i_1 = 0.008 \text{ A}$$

$$\begin{aligned} \text{Total power consumed} &= V \cdot I \\ &= 24 \cdot (0.004 + 0.004 + 0.008) \times 1000 \\ &= 384 \text{ W} \end{aligned}$$

2. 2) abcfa loop:

$$E_1 - I_1 r_1 + I_2 r_2 - E_2 = 0$$

$$1.5 - I_1(0.25) + I_2(0.25) - 1.5 = 0$$

$$I_2(0.25) = I_1(0.25)$$

$$I_2 = I_1 \quad (1)$$

fcdef loop:

$$E_2 - I_2 r_2 - IR = 0$$

$$1.5 - I_2(0.25) - (I_1 + I_2)50 = 0$$

$$1.5 - I_2(0.25) - (2I_2)50 = 0$$

$$-I_2(0.25) - (2I_2)50 = -1.5$$

$$-0.25I_2 - 100I_2 = -1.5$$

$$-100.25I_2 = -1.5$$

$$I_2 \approx 0.01496 \text{ A}$$

so that means that $I_1 \approx 0.01496 \text{ A}$

then $I = I_1 + I_2$

$$I \approx 0.029925 \text{ A}$$

known:

$$E = 1.5 \text{ V}$$

$$r = 0.25 \Omega$$

$$R = 50 \Omega$$

R needs to be 1.43Ω .

$$I = I_2 + I_1$$

$$b) I = \frac{q}{t} \Rightarrow t = \frac{q}{I}$$

known:

$$q = 2.5 \text{ A hr}$$

$$t = \frac{2.5 \text{ A hr}}{0.029925 \text{ A}}$$

$$t \approx 83.54166397 \text{ hr}$$

Chapter 11

1. a) positive

b) It is weird because the particle has the mass of an electron. It is like a contradiction because an electron is negatively charged. Which is why it is strange.

c) known:

$$B = 0.05 \text{ T} \quad V = 10^6 \text{ m/s} \quad \text{particle} = +1.6 \times 10^{-19} \text{ C}$$

$$F = q\vec{v} \times \vec{B}$$

$$F = 1.6 \times 10^{-19} \cdot 10^6 \cdot 0.05$$

$$F = 8 \times 10^{-15} \text{ N}$$