

# Wednesday Reading Assessment: Unit 5, Field Induction and Inductance

Prof. Jordan C. Hanson

April 22, 2020

## 1 Memory Bank

- $\epsilon = -L \frac{dI}{dt}$  ... Faraday's law with induction,  $L$ . Think of this as the change in voltage across an inductor.
- Kirchoff's loop rule: the sum of all changes in voltage around a loop in a circuit must be zero.

## 2 RL Circuits

1. Consider the DC circuit in Fig. 1. There is a battery emf  $\epsilon$  connected to a resistor  $R$  and an inductor  $L$  via switch 1. Switch 2 simply connects  $L$  and  $R$ . Suppose we observe the current through the circuit when switch 1 is closed to be

$$i(t) = \frac{\epsilon}{R} (1 - \exp(-t/\tau)) \quad (1)$$

(a) Based on Kirchoff's loop rule, write down the differential equation that describes the loop when switch 1 is closed. Note that  $\tau = L/R$ . (b) Plug in Eq. 1 into your differential equation to see if it works.

2. Now we repeat this exercise, but with switch 2 closed and switch 1 opened, after the circuit reaches equilibrium ( $t \gg \tau$ , when switch 1 was closed). The equation is observed to be

$$i(t) = \frac{\epsilon}{R} \exp(-t/\tau) \quad (2)$$

What formula do we obtain when we apply Kirchoff's loop rule? (This is now the situation in part (c) of Fig. 1).

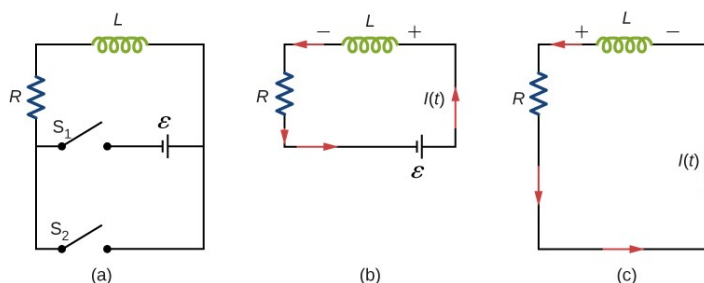


Figure 1: A circuit diagram of a DC emf with a resistor, inductor, and two switches.