

# Monday Reading Assessment: Unit 2, Ohm's Law and Batteries, Kirchhoff's Rules

Prof. Jordan C. Hanson

March 23, 2020

## 1 Memory Bank

- $i_{\text{in}} = i_{\text{out}}$  ... Kirchhoff's junction rule.
- $\epsilon_1 + \epsilon_2 + \epsilon_3 + \dots = 0$  ... Kirchhoff's loop rule.

## 2 Kirchhoff's Rules Tutorial

1. Recall the Kirchhoff's Rules tutorial video 1. We solved for the current  $i_1$  in Fig. 1. (a) What is  $i_2$ ? Once you find  $i_2$ , find  $i_3$  using the junction rule. What does the sign of  $i_3$  tell us about the lower battery? (b) Suppose the emf of battery 2 was raised to  $\epsilon_2 = 12$  V, and we observe that  $i_1 = 1.2$  A and  $i_2 = 1.2$  A. What is  $i_3$ ?

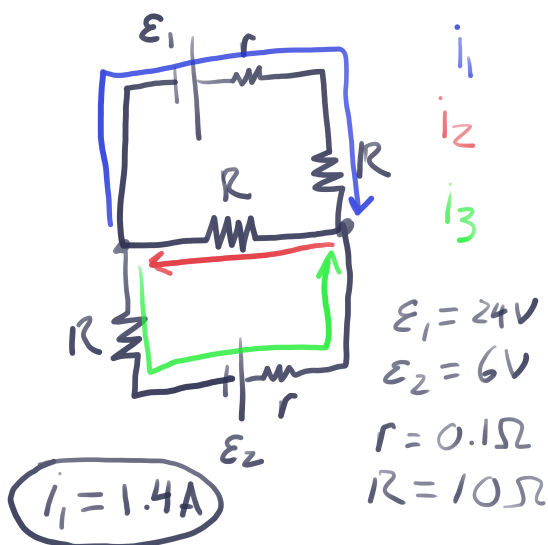


Figure 1: The circuit from Kirchhoff tutorial video 1. Two batteries with internal resistances  $r$  are connected to a circuit with resistors  $R$ .