

# Study Guide for Midterm 2

Dr. Jordan Hanson - Whittier College Dept. of Physics and Astronomy

March 23, 2020

## 1 Memory Bank

1.  $\vec{F} = k \frac{q_1 q_2}{r^2} \hat{r}$  ... Coulomb Force
2.  $k = 9 \times 10^9 \text{ N C}^{-2} \text{ m}^2$  ... Remember  $k = 1/(4\pi\epsilon_0)$ .
3.  $q_e = 1.6 \times 10^{-19} \text{ C}$  ... Charge of an electron/proton
4.  $\vec{F} = q\vec{E}$  ... Electric field and charge
5.  $\vec{E}(z) = \frac{\sigma}{\epsilon_0} \hat{z}$  ... Electric field of two oppositely charge planes each with charge density  $\sigma$
6.  $\epsilon_0 \approx 8.85 \times 10^{-12} \text{ F/m}$
7.  $dE = \int k dq / r^2$  ... Remember that  $dq$  takes the form below
8.  $dq = \lambda dx$  ... Linear charge density (C/m)
9.  $\vec{E} \cdot \vec{A} = Q_{enc} / \epsilon_0$  ... Gauss' Law, constant electric field over the surface area.
10.  $U = q\Delta V$  ... Potential energy and voltage
11. 1 eV: an electron-Volt is the amount of energy one electron gains through 1 V.
12.  $V(r) = k \frac{q}{r}$  ... Voltage of a point charge
13.  $\vec{E} = -\frac{\Delta V}{\Delta x}$  ... E-field is the slope or change in voltage with respect to distance
14.  $V(x) = -Ex + V_0$  ... Voltage is linear between two charge planes
15.  $Q = CV$  ... Definition of capacitance
16.  $C = \frac{\epsilon_0 A}{d}$  ... Capacitance of a parallel plate capacitor
17.  $C_{tot}^{-1} = C_1^{-1} + C_2^{-1}$  ... Adding two capacitors *in series*.
18.  $C_{tot} = C_1 + C_2$  ... Adding two capacitors *in parallel*.
19.  $i(t) = dQ/dt$  ... Definition of current.
20.  $v_d = i/(nqA)$  ... Charge drift velocity in a current  $i$  in a conductor with number density  $n$  and area  $A$ .
21.  $R_{tot}^{-1} = R_1^{-1} + R_2^{-1}$  ... Adding two capacitors *in parallel*.
22.  $R_{tot} = R_1 + R_2$  ... Adding two capacitors *in series*.
23.  $\Delta V = IR_{tot}$ ,  $\vec{J} = \sigma \vec{E}$  ... Versions of Ohm's Law. ( $\vec{J}$  is the current density with units of Amps per meter-squared).
24.  $P = IV$  ... Relationship between power, current, and voltage.
25.  $V_C(t) = \epsilon_1 (1 - \exp(-t/\tau))$  ... voltage across the capacitor in an RC series circuit. The time constant  $\tau = RC$ .
26.  $i(t) = \frac{\epsilon_1}{R} \exp(-t/\tau)$  ... Current in an RC series circuit.
27.  $i_{in} = i_{out}$  ... Kirchhoff's junction rule.
28.  $\epsilon_1 + \epsilon_2 + \epsilon_3 + \dots = 0$  ... Kirchhoff's loop rule.
29.  $\vec{F} = q\vec{v} \times \vec{B}$  ... The Lorentz force on a charge  $q$  with velocity  $\vec{v}$  in a magnetic field  $\vec{B}$ .
30.  $\vec{F} = I\vec{L} \times \vec{B}$  ... The Lorentz force on a conductor of length  $\vec{L}$  carrying a current  $I$  in a magnetic field  $\vec{B}$ .

## 2 Chapter 9: Current and Resistance

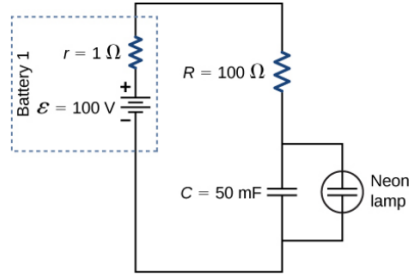


Figure 1: This type of circuit is called a relaxation oscillator.

- Fig. 1 shows a *relaxation oscillator*. The RC circuit charges, and once the capacitor voltage reaches 50 V, the neon lamp activates and completely discharges the capacitor. The process then repeats. (a) Are the internal battery resistance and resistor  $R$  in series or parallel? Simplify the circuit and apply Kirchhoff's loop rule to the circuit. Remember that  $V_C = Q/C$  is the voltage across the capacitor. (b) Take the derivative of both sides to obtain an equation involving the current and the derivative of the current. (c) What is  $i(t)$ , the current as a function of time? (Solve the differential equation in part b). (d) Using  $V_C = Q/C$ , find an equation for  $V_C(t)$ , the voltage as a function of time across the capacitor. When does  $V_C = 50$  V?

- Imagine an *alternating current* (AC) system, as opposed to the DC systems we normally consider. In AC circuits, the voltage follows a form

$$V(t) = V_0 \sin(2\pi ft + \phi) \quad (1)$$

The wall outlets in the USA have  $f = 60$  Hz and  $V_0 = 120$  V. *We have the freedom to choose  $\phi$  in this example, much like choosing the zero-point of voltage.* (a) If a  $5 \text{ k}\Omega$  resistor is placed across this voltage, what will the maximum current be? (b) What is the maximum power in the resistor? (c) Another way to write power is  $P = V^2/R$ . What is the power consumed by the resistor 100 ms after being connected?

- Three identical resistors  $R$  are connected *in parallel*, and powered by an adjustable voltage source. The voltage and *total current* measurements are shown below. Determine the value of  $R$ .

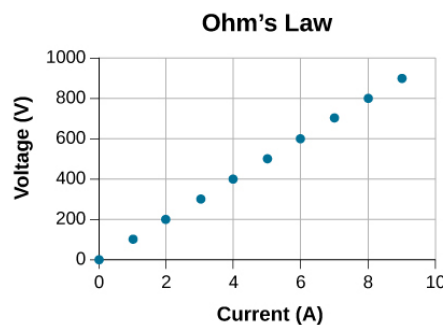


Figure 2: A graph of voltage versus .

### 3 Chapter 10: Direct-Current (DC) Circuits

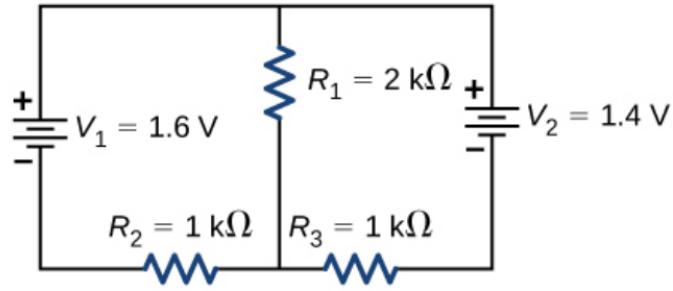


Figure 3: A circuit with two batteries and three resistors.

1. Solve for the current through each of the three resistors in Fig. 3.
2. Suppose a calculator with total resistance  $R$  needs between 2.5 and 3.3 volts to operator. Two AA batteries with  $\epsilon = 1.5\text{V}$  and  $r = 0.25\Omega$  are connected (Fig. 4) in series to form a  $\epsilon = 3.0\text{ V}$  battery. (a) If the calculator has an effect resistance of  $R = 50\Omega$ , what is the current flow? (b) If the batteries each have a charge  $q = 2.5\text{ A hr}$ , how long will the current flow?

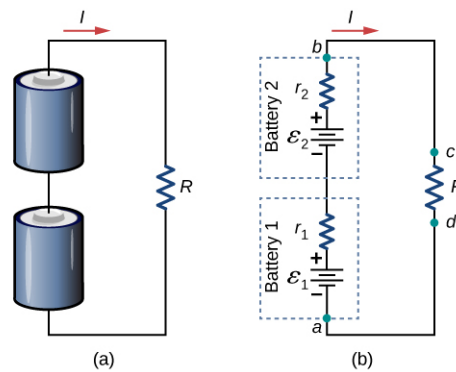


Figure 4: Two AA batteries are connected *in series* to power a calculator represented by  $R$ . (a) The batteries are connected in series. (b) A circuit diagram representing the circuit in (a).

## 4 Chapter 11: Magnetic Forces and Fields

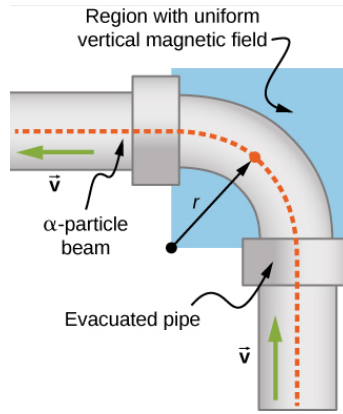


Figure 5: The trajectory of a beam of alpha-particles with  $m = 6.64 \times 10^{-27}$  kg and charge  $q = 3.2 \times 10^{-19}$  C is curved 90 degrees to the left.

1. **Practice with cross-products.** Evaluate the following cross-products:

- $\vec{v}_1 = 4\hat{i} + 4\hat{j}$ ,  $\vec{v}_2 = -2\hat{i} - 2\hat{j}$ .  $\vec{v}_1 \times \vec{v}_2 =$
- $\vec{v}_1 = 4\hat{i} - 4\hat{j}$ ,  $\vec{v}_2 = 2\hat{i} - 2\hat{j}$ .  $\vec{v}_1 \times \vec{v}_2 =$
- $\vec{v}_1 = -2\hat{i} + 2\hat{j}$ ,  $\vec{v}_2 = -3\hat{i} + 2\hat{j}$ .  $\vec{v}_1 \times \vec{v}_2 =$
- $\vec{v}_1 = -2\hat{i} - 2\hat{j} + \hat{k}$ ,  $\vec{v}_2 = 3\hat{i} + 2\hat{j} - \hat{k}$ .  $\vec{v}_1 \times \vec{v}_2 =$

2. A research group is investigating short-lived radioactive isotopes. They need to design a way to transport alpha-particles (helium nuclei) from where they are made to a place where they will collide with another material to form an isotope. The alpha-particles form a beam (Fig. 5) that bends through a 90-degree region with a uniform magnetic field of 0.050 T. (a) In what direction should the magnetic field be applied? (b) How much time does it take the alpha-particles to traverse the uniform magnetic field region?