

Study Guide for Midterm 2 for Calculus-Based Physics: Electricity and Magnetism, with Answers

Dr. Jordan Hanson - Whittier College Dept. of Physics and Astronomy

April 13, 2019

1 Equations and constants

1. Kirchhoff's Rules: 1) $I_{in} + I_{out} = 0$ (Junction Rule) 2) $\sum_{loop} V_i = 0$ (Loop Rule)
2. Ohm's Law: $V = IR$
3. Power from current: $P = IV$
4. Voltage in an RC across the capacitor: $V(t) = \epsilon(1 - \exp(-t/\tau))$, where ϵ is the battery voltage and $\tau = RC$.
5. Centripetal force: $F_C = mv^2/r$.
6. Magnetic torque: $\vec{\tau}_B = \vec{\mu} \times \vec{B}$
7. Magnitude of torque: $|\vec{\tau}_B| = \mu B \sin \theta$
8. Magnetic dipole moment: $\vec{\mu} = I\vec{A}$ (the current times the area vector)
9. Magnetic field at the center of a current-carrying loop: $\vec{B} = (\mu_0 I)/(2R)\hat{z}$, if the current is in the x-y plane.
10. Ampere's Law: $\int \vec{B} \cdot d\vec{s} = \mu_0 I_{enc}$ which is $BS = \mu_0 I_{enc}$ for simple cases where B is constant around the path.
11. Magnetic permeability: $\mu_0 = 4\pi \times 10^{-7} \text{ T m A}^{-1}$

2 Exercises

1. Chapter 10: DC Circuits and Kirchhoff's Rules

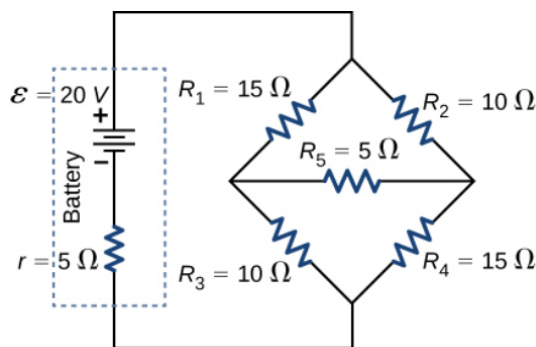


Figure 1: A circuit with five resistors powered by a battery with internal resistance.

- (a) What is the current flowing from the battery in Fig. 1? What is the total power consumption?
The current from the battery is $I = 1.17 \text{ A}$, and the total power consumption is 23.4 W .
- (b) Solve algebraically for the five currents in Fig. 2. Remember to use the *junction rule* and the *loop rule*.
Hint:

- Loop 1: $I_1 R_1 - I_2 R_2 + V_1 = 0$
- Loop 2: $I_2 R_2 + I_3 R_3 - I_4 R_4 - V_2 = 0$
- Loop 3: $-I_5 R_5 + V_2 = 0$
- Junction 1: $I_1 + I_3 = I_2$
- Junction 2: $I_2 + I_5 = I_4$

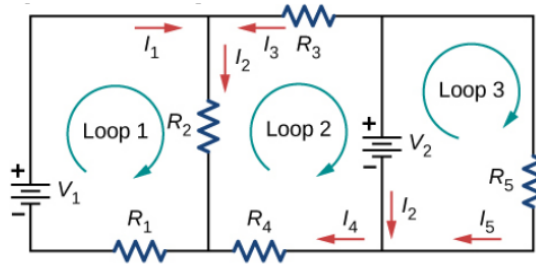


Figure 2: A circuit consisting of two batteries and five resistors.

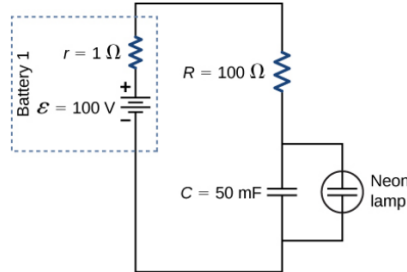


Figure 3: This type of circuit is called a relaxation oscillator.

- (c) Figure 3 shows a *relaxation oscillator*. The RC circuit charges, and once the capacitor voltage reaches 50 V, the neon lamp lights and completely discharges the capacitor. The process then repeats. How long between neon lamp flashes?

Let $\tau = RC$. **It can be shown that the voltage across the capacitor is given by**

$$V(t) = \epsilon (1 - \exp(-t/\tau)) \quad (1)$$

We solve for the time:

$$t = -\tau \ln(1 - V/\epsilon) \quad (2)$$

Plugging in the numbers, we find that each 3.5 seconds, the voltage will be 50 V. Thus, the lamp flashes every 3.5 seconds.

2. Chapter 11: Magnetic forces and fields

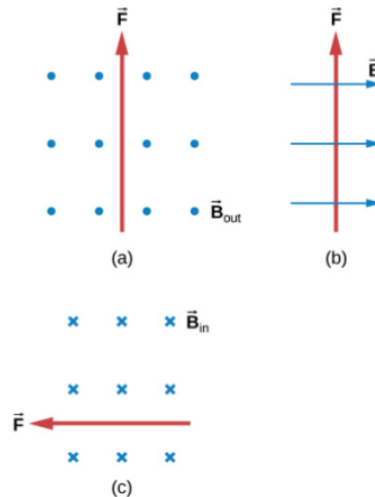


Figure 4: Each diagram depicts the force on a negatively-charged particle in a B-field.

- (a) Determine the velocity of a negatively-charged particle in Fig. 4 (a)-(c).

- (a): To the right.
- (b): In to the page.
- (c): Down.

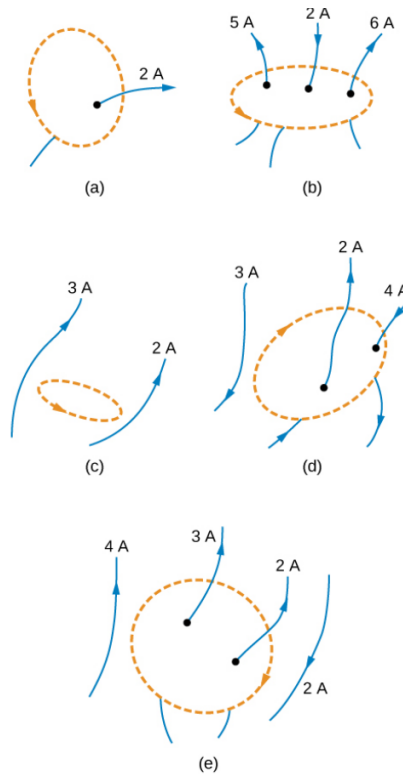


Figure 5: Several current arrangements with closed line integrals.

- (b) A cosmic-ray electron moves at 6×10^6 m/s perpendicular to Earth's magnetic field at an altitude where the field strength is 1.0×10^{-5} T. What is the radius of the circular path the electron follows? Show that the *angular velocity* ω of the electron around the magnetic field lines is related to the q/m ratio by $\omega/B = q/m$. **We find the radius by setting the Lorentz force equal to the centripetal force.**

$$r = \frac{mv}{qB} \quad (3)$$

The result turns out to be ≈ 3.4 m.

- (c) What is the maximum torque on a 150-turn circular loop of wire with radius 8.0 cm that carries a 50.0-A current in a 1.60 T B-field?

The simplified formula turns out to be

$$\tau = NIAB = 150 \times 50 \times \pi \times 0.08^2 \times 1.6 \approx 240 \quad (4)$$

Thus, 240 N m of torque.

3. Chapter 12: Sources of Magnetic Fields

- (a) What is the magnetic field created by the loops in the previous problem, at the center of the loops? What is the *total* magnetic moment of the loops?

The magnetic field formula follows from the Biot-Savart law:

$$B = \frac{N\mu_0 I}{2R} = \frac{150 \times 4\pi \times 10^{-7} \times 50.0}{2 \times 0.08} \approx 590G \quad (5)$$

About 590 Gauss.

- (b) Using Ampère's Law, re-derive the equation for a magnetic field due to a long straight wire. Now model a lightning bolt as a long straight wire. A typical current in a lightning bolt is 10^4 A. Estimate the magnetic field 1 m from the bolt.

$BS = \mu_0 I$, so

$$B = \frac{\mu_0 I}{S} = \frac{\mu_0 I}{2\pi R} \quad (6)$$

Using the right hand rule gives the direction. Plugging in the numbers, we find about 20 Gauss.

- (c) Evaluate $\oint \vec{B} \cdot d\vec{l}$ for cases (a)-(e) in Fig. 5.

The basic concept of Ampere's Law is that this integral is proportional to the total enclosed current. The constant of proportionality is μ_0 .