

## MidTerm #2

①  $R = 1000 \Omega$

$100 \times 10^{-6} = 1000 (C)$

$\tau = RC < 100 \mu s$

$\uparrow$  time     $\uparrow$  Resis     $\nwarrow$  capacitance

$C = 1 \times 10^{-7} F$

b) No, it wouldn't be difficult because there are capacitors smaller than that value

c)  $V_c(t) = V_0 (1 - e^{-t/\tau})$

$30 \times 10^{-3} = 60 \times 10^{-3} (1 - e^{-t/100 \mu s})$

$\frac{1}{2} = 1 - e^{-t/100} \rightarrow \frac{1}{2} = e^{-t/100} \rightarrow \ln \frac{1}{2} = \ln e^{-t/100}$

$\ln \frac{1}{2} = \frac{-t}{100} \rightarrow t = -100 \ln \frac{1}{2} \rightarrow \boxed{t = -100 \times 10^{-6} \ln(\frac{1}{2})}$

②  $v(t) = V_0 \sin(2\pi f t + \phi)$      $f = 60 \text{ Hz}$      $V_0 = 120 \text{ V}$

a)  $\phi = 0 \rightarrow v(t) = V_0 \sin(2\pi f t)$

$0 = V_0 \sin(2\pi f t)$

$+ K \frac{1}{120}$

$0 = 120 \sin(2\pi(60)t) \rightarrow 0 = 120 \sin(120\pi t)$

$0 = \sin(120\pi t)$


$\text{wavelength} = \frac{2\pi}{120\pi} = \frac{1}{60} \cdot \frac{1}{2} = \frac{1}{120}$

$\boxed{t = \frac{1}{120} \text{ sec}}$

b)  $P = IV$      $V = IR \rightarrow I = V/R$

$P_{\text{MAX}} = \frac{V_{\text{MAX}}^2}{R_{\text{MAX}}} = \frac{(120)^2}{1000 \Omega} = \boxed{14.4 \text{ W}}$

c)  $P \propto V$

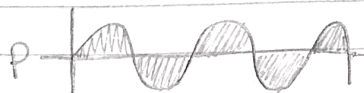

Avg. power = 0 W

③ Fridge : 3 A , 110 V

Lamp : 100 W

Light : 60 W

Random : 3 W

$$.2 \frac{\text{dollars}}{\text{kWhr}} = .2 \frac{\text{dollars}}{1000 \text{ Whr}}$$

360 hrs

12 hr  
day

1 month  
(30 days)


$$P = IV = 3(110) = 330 \text{ W}$$

$$P_{\text{Tot}} = 330 + 100 + 60 + 3 = 493 \text{ W}$$


$$\frac{.2}{1000} \frac{1}{\text{Whr}} \cdot \frac{360 \text{ hr}}{1} \cdot \frac{493 \text{ W}}{1} = \$35,496$$

④

a)

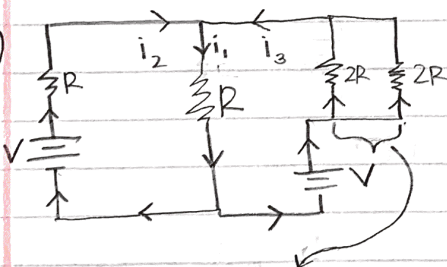

simplify

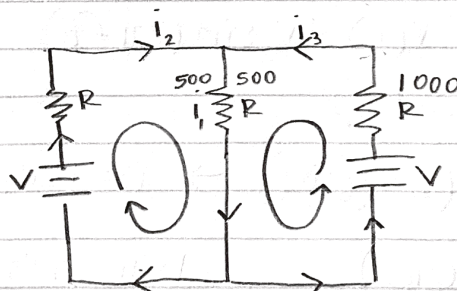

$$i_2 + i_3 = i_1$$

$$R_{\text{Tot}} = \frac{1}{2000} + \frac{1}{2000} = \frac{2}{2000} = 1000 \Omega$$

$$V = 12 \text{ V}$$

$$R_{\text{Tot}} = 1500 \Omega$$

$$V = IR$$

$$i_3 = 0.008 \text{ A}$$

$$i_3 = i_2 = 0.008 \text{ A}$$

$$i_1 = 0.008 + 0.008 = 0.016 \text{ A}$$

$$P = I^2 R$$

$$P_1 = (.008)^2 (1000) = 0.064 \text{ W}$$

$$P_2 = (.016)^2 (1000) = 0.256 \text{ W}$$

$$P_3 = (.008)^2 (1000) = 0.064 \text{ W}$$


$$P_{\text{Tot}} = P_1 + P_2 + P_3$$

$$P_{\text{Tot}} = 0.384 \text{ W}$$

⑤ R btwn. 1.4 - 2 V

$$\mathcal{E} = 1.5 \text{ V}$$

$$r = 0.25 \Omega$$

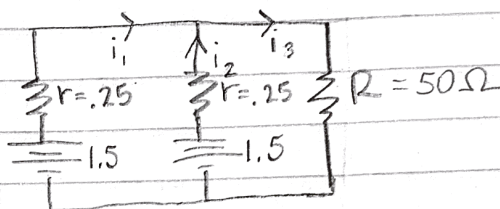

$$R_{\text{Tot}} = \frac{1}{.25} + \frac{1}{.25} = 0.125 \Omega + 50 \Omega = 50.125 \Omega$$

$$V_{\text{Tot}} = 1.5 \text{ V} + 1.5 \text{ V} = 3 \text{ V}$$

$$V = IR \rightarrow I = \frac{V}{R} = \frac{3 \text{ V}}{50.125 \Omega} = 0.06 \text{ A}$$

b)  $q = 2.5 \text{ A hr}$      $I = 0.06 \text{ A}$

$$\frac{q}{I} = t = \frac{2.5 \text{ A hr}}{0.06 \text{ A}} = 41.7 \text{ hr}$$

⑥ a) The particle is positive

← ⊗ Moving to left  
↑ Right hand rule

b) It is strange because the particle has the mass of an electron, yet it's positive not negative

c)  $F = qv \times B = (1.6 \times 10^{-19})(10^6)(0.05)$

$$F = 8 \times 10^{-15} \text{ N}$$

Direction: moving to left (negative x-direction)