

Study Guide for Midterm 2 for Calculus-Based Physics: Electricity and Magnetism

Dr. Jordan Hanson - Whittier College Dept. of Physics and Astronomy

April 8, 2019

1. Chapter 10: DC Circuits and Kirchhoff's Rules

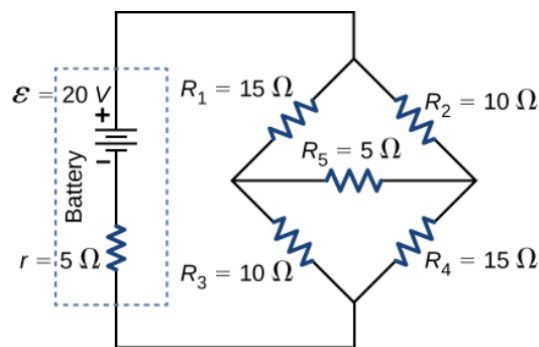


Figure 1: A circuit with five resistors powered by a battery with internal resistance.

- (a) What is the current flowing from the battery in Fig. 1? What is the total power consumption?

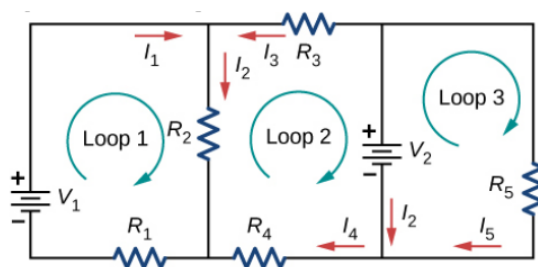


Figure 2: A circuit consisting of two batteries and five resistors.

- (b) Solve algebraically for the five currents in Fig. 2. Remember to use the *junction rule* and the *loop rule*.

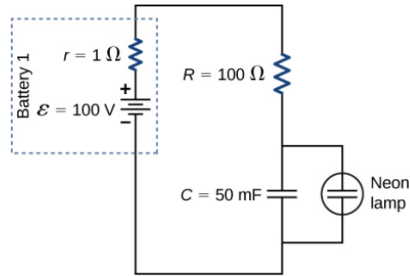


Figure 3: This type of circuit is called a relaxation oscillator.

- (c) Figure 3 shows a *relaxation oscillator*. The RC circuit charges, and once the capacitor voltage reaches 50 V, the neon lamp lights and completely discharges the capacitor. The process then repeats. How long between neon lamp flashes?

2. Chapter 11: Magnetic forces and fields

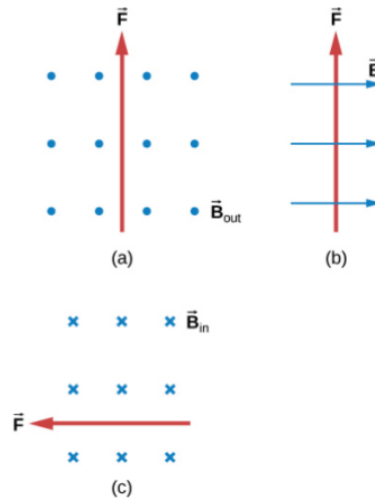


Figure 4: Each diagram depicts the force on a negatively-charged particle in a B-field.

- (a) Determine the velocity of a negatively-charged particle in Fig. 4 (a)-(c).
- (b) A cosmic-ray electron moves at 6×10^6 m/s perpendicular to Earth's magnetic field at an altitude where the field strength is 1.0×10^{-5} T. What is the radius of the circular path the electron follows? Show that the *angular velocity* ω of the electron around the magnetic field lines is related to the q/m ratio by $\omega/B = q/m$.
- (c) What is the maximum torque on a 150-turn circular loop of wire with radius 8.0 cm that carries a 50.0-A current in a 1.60 T B-field?

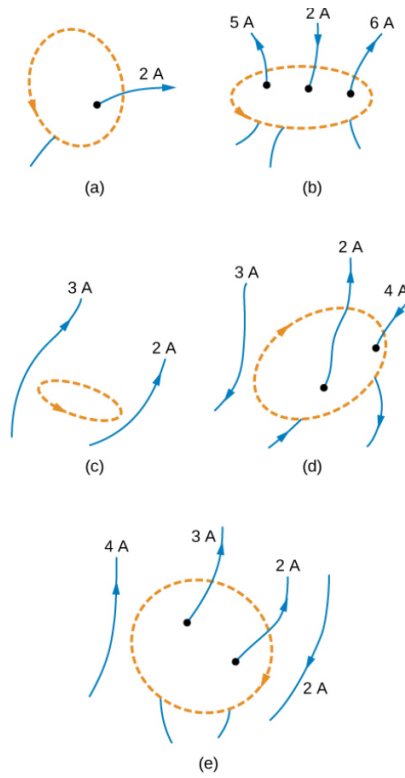


Figure 5: Several current arrangements with closed line integrals.

3. Chapter 12: Sources of Magnetic Fields

- (a) What is the magnetic field created by the loops in the previous problem, at the center of the loops? What is the *total* magnetic moment of the loops?
- (b) Using Ampère's Law, re-derive the equation for a magnetic field due to a long straight wire. Now model a lightning bolt as a long straight wire. A typical current in a lightning bolt is 10^4 A. Estimate the magnetic field 1 m from the bolt.
- (c) Evaluate $\oint \vec{B} \cdot d\vec{l}$ for cases (a)-(e) in Fig. 5.